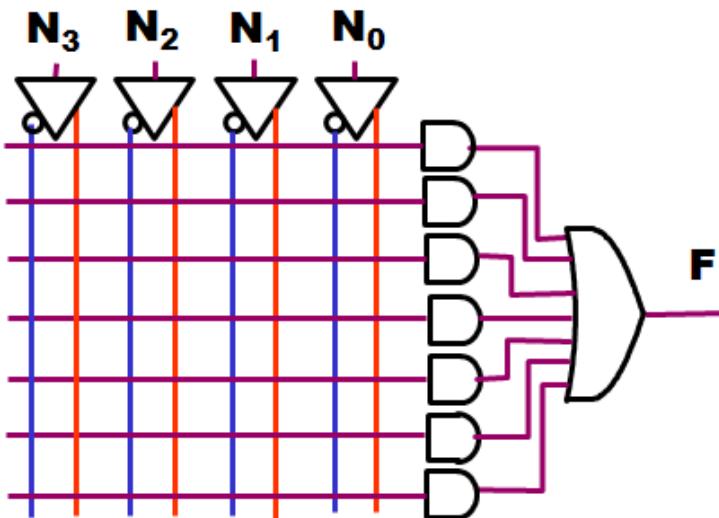


Eksempel – Primtals detektor


Lav et kredsløb der på grundlag af et 4-bit input bestemmer om N (et tal mellem 0 og 15) er et primtal
 $F=1$ hvis N er et primtal ellers $F=0$

**Sandhedstabel for
Primtal-Detektor**



**Logik til primtalsdetektor
uden reduktion**
Se Wakerly figur 4-18 side 206

N_3	N_2	N_1	N_0	F
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

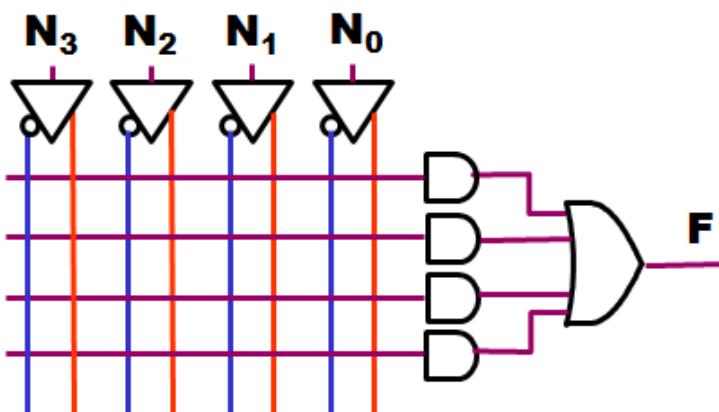

N_3N_2	00	01	11	10
N_1N_0	0 0	0 1	1 1	1 0
0 0	0	4	12	8
0 1	1	5	13	9
1 1	3	7	15	11
1 0	2	6	14	10

**Logik til primtalsdetektor
efters reduktion**
Se Wakerly figur 4-25 side 212

$$F =$$

```

architecture prime2_arch of prime is
  signal N3L_N0, N3L_N2L_N1, N2L_N1_N0, N2_N1L_N0: STD_LOGIC;
begin
  N3L_N0      <= not N(3)                                     and N(0);
  N3L_N2L_N1 <= not N(3) and not N(2) and      N(1);
  N2L_N1_N0  <=           not N(2) and      N(1) and N(0);
  N2_N1L_N0  <=           N(2) and not N(1) and N(0);
  F <= N3L_N0 or N3L_N2L_N1 or N2L_N1_N0 or N2_N1L_N0;
end prime2_arch;

```


Wakerly tabel 5-37 dataflow VHDL
Primtals detektor med boolske udtryk

```

architecture prime3_arch of prime is
  signal N3L_N0, N3L_N2L_N1, N2L_N1_N0, N2_N1L_N0: STD_LOGIC;
begin
  N3L_N0      <= '1' when N(3)= '0' and N(0)= '1' else
                '0';
  N3L_N2L_N1 <= '1' when N(3)= '0' and N(2)= '0' and N(1)= '1' else
                '0';
  N2L_N1_N0  <= '1' when N(2)= '0' and N(1)= '1' and N(0)= '1' else
                '0';
  N2_N1L_N0  <= '1' when N(2)= '1' and N(1)= '0' and N(0)= '1' else
                '0';
  F <= N3L_N0 or N3L_N2L_N1 or N2L_N1_N0 or N2_N1L_N0;
end prime3_arch;

```

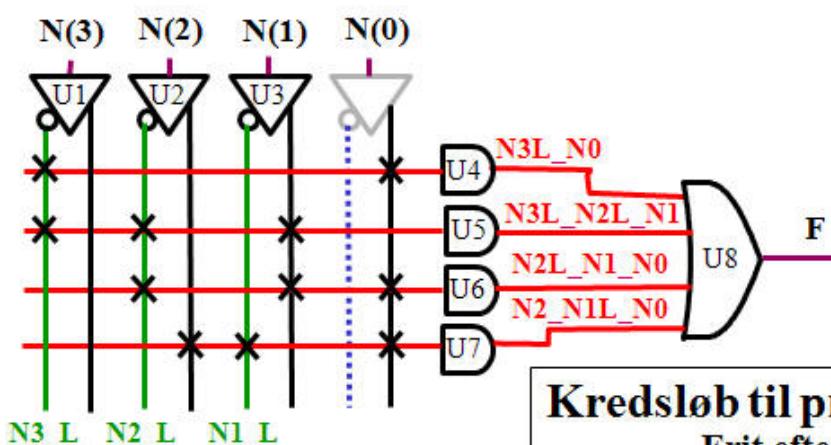Wakerly tabel 5-38 dataflow VHDL
Primtals detektor med **when else** sætninger



Kredsløb til primtalsdetektor
Frit efter Wakerly

```

architecture prime4_arch of prime is
begin
    with N select
        F <= '1' when "0001",
        '1' when "0010",
        '1' when "0011" | "0101" | "0111" | "1011" | "1101",
        '0' when others;
end prime4_arch;

```

Wakerly tabel 5-40
with sætning med
select signal angivelse

```

function CONV_INTEGER ( X: STD_LOGIC_VECTOR ) return INTEGER is
    variable RESULT: INTEGER;
begin
    RESULT := 0;
    for i in X'range loop
        RESULT := RESULT * 2;
        case X(i) is
            when '0' | 'L' => null;
            when '1' | 'H' => RESULT := RESULT + 1;
            when others => null;
        end case;
    end loop;
    return RESULT;
end CONV_INTEGER;

```

Wakerly tabel 5-25 function der konverterer
en *STD_LOGIC_VECTOR* til en *INTEGER*

```

architecture prime5_arch of prime is
begin
    with CONV_INTEGER(N) select
        F <= '1' when 1 | 2 | 3 | 5 | 7 | 11 | 13,
        '0' when others;
end prime5_arch;

```

Wakerly tabel 5-41
with sætning med
lettere læselig kode

```
architecture prime6_arch of prime is
begin
```

```
process (N)
variable N3L_N0, N3L_N2L_N1, N2L_N1_N0, N2_N1L_N0: STD_LOGIC;
begin
  N3L_N0      := not N(3)                                and N(0);
  N3L_N2L_N1  := not N(3) and not N(2) and N(1);
  N2L_N1_N0   := not N(2) and N(1) and N(0);
  N2_N1L_N0   := N(2) and not N(1) and N(0);
  F <= N3L_N0 or N3L_N2L_N1 or N2L_N1_N0 or N2_N1L_N0;
end process;
```

```
end prime6_arch;
```

Wakerly tabel 5-43 Proces med boolske udtryk

```
architecture prime7_arch of prime is
begin
```

```
process (N)
variable NI: INTEGER;
begin
  NI := CONV_INTEGER (N);
  if NI=1 or NI=2 then
    F <= '1';
  elsif NI=3 or NI=5 or NI=7 or NI=11 or NI=13 then
    F <= '1';
  else
    F <= '0';
  end if;
end process;
```

```
end prime7_arch;
```

Wakerly tabel 5-45
Proces med if sætning

```
architecture prime8_arch of prime is
begin
```

```
process (N);
begin
  case CONV_INTEGER (N) is
    when 1 => F <= '1';
    when 2 => F <= '1';
    when 3 | 5 | 7 | 11 | 13 => F <= '1';
    when others        => F <= '0';
  end case;
end process;
```

```
end prime8_arch;
```

Wakerly tabel 5-47
Proces med case
sætning

```

entity prime9 is
  port ( N: in STD_LOGIC_VECTOR ( 7 downto 0);
          F: out STD_LOGIC);
architecture prime9_arch of prime9 is
begin
  process (N)
    variable NI: INTEGER;
    variable Prime: BOOLEAN;
  begin
    NI := CONV_INTEGER ( N );
    Prime := true;
    if NI=1 or NI=2 then
      null;
    else
      for i in 2 to 253 loop
        if (NI mod i=0) and (NI/i) then
          prime := false;
          exit;
        end if;
      end loop;
    end if;
    if Prime then
      F <= '1';
    else
      F <= '0';
    end if;
  end process;
end prime9_arch;

```

Wakerly tabel 5-50
Primtals-detektor baseret
på et "højniveau-program"

```

entity Prime8 is
  Generic( Max: Natural := 6);
  Port ( N : in STD_LOGIC_VECTOR (Max downto 0);
         Prime : out STD_LOGIC);
end Prime8;

```

```

36   architecture Behavioral of Prime8 is
37   begin
38   -- The process finds Primes by the the principles
39   -- of Eratostens Sive
40   Process(N)
41     type tabel is array (0 to 2**Max-1) of boolean;
42     variable Primtal,Tal: tabel;
43     variable Ni,j: integer range 0 to 2**Max;
44   begin
45     ----- Fill Tal with all numbers 0 to 2**Max
46     for i in Primtal'Range loop
47       Primtal(i) := False; -- Clear the Prime sive
48       Tal(i) := True;
49     end loop;
50     ----- Remove 0,1 and set 2 as a Prime
51     Tal(0) := False;
52     Tal(1) := False;
53     Primtal(1) := True;
54     -- The Next (lowest) number will be a Prime
55     for i in 2 to 2**Max-1 loop
56       if Tal(i) then
57         Primtal(i) := True; -- Set as Prime
58         j := i;
59         while j<2**Max loop
60           Tal(j) := False; -- Remove Multipla
61           j := j+i;
62         end loop;
63         end if;
64       end loop;
65
66     Ni := conv_integer(N); -- Now decide if
67     if Primtal(Ni) then -- N is a Prime number
68       Prime <= '1';
69     else
70       Prime <= '0';
71     end if;
72   end process;
73 end Behavioral;

```